## SPICE Model – MOS6020


This lumped-element (SPICE) model data simulates the frequency-dependent behavior of Coilcraft power inductors within the frequency range shown in the accompanying table for each individual inductor.

The data represents de-embedded measurements, as described below. Effects due to different customer circuit board traces, board materials, ground planes or interactions with other components are not included and can have a significant effect when comparing the simulation to measurements of the inductors using other production verification instruments and fixtures.
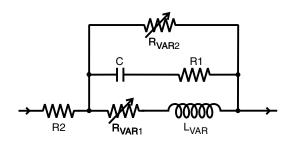
## **Lumped Element Modeling Method**

Measurements were made using a 50 Ohm impedance analyzer. Fixture compensation was performed to remove fixture effects. No DC bias current was applied in any of the measurements. The lumped element values were determined by optimizing the simulation model to an average of the measurements. This method results in a model that represents as closely as possible the typical frequency-dependent behavior of the component within the model frequency range.

The equivalent lumped element model schematic is shown below. Each model should be analyzed only at the input and output ports. Conclusions based on individual lumped element values may be erroneous.



The value of the frequency-dependent variable resistor  $R_{VAB1}$  is calculated from:

$$R_{VAR1} = k1 * \sqrt{f}$$

- k1 is shown for each value in the accompanying table.
- · f is the frequency in Hz
- R<sub>VAR1</sub> is the resistance in Ohms

The value of the frequency-dependent variable resistor  $R_{VAR2}$  is calculated from:

$$R_{VAR2} = k2 * \sqrt{f}$$

- k2 is shown for each value in the accompanying table.
- f is the frequency in Hz
- R<sub>VAR2</sub> is the resistance in Ohms

The value of the frequency-dependent inductance  $L_{VAR}$  is calculated from:

$$L_{VAR} = k3 - k4 * LOG (k5 * f)$$

- k3, k4, and k5 are shown in the accompanying table.
- f is the frequency in Hz
- L<sub>VAR</sub> is the inductance in μH

## Disclaimer

Coilcraft makes every attempt to provide accurate measurement data and software, representative of our components, in a usable format. Coilcraft, however, disclaims all warrants relating to the use of its data and software, whether expressed or implied, including without limitation any implied warranties of merchantability or fitness for a particular purpose. Coilcraft cannot and will not be liable for any special, incidental, consequential, indirect or similar damages occurring with the use of the data and/or software.



## SPICE Model for Coilcraft MOS6020 Power Inductors

		ncy limit el (MHz)					L <sub>VAR</sub> Coefficients				
Part number	Lower	Upper	R1 (Ω)	R2 (Ω)	C (pF)	k1	k2	k3	k4	k5	
MOS6020-222	0.1	100	30	0.035	0.850	1.00E-08	0.247	2.2	0.005	9.20E-06	
MOS6020-332	0.1	100	120	0.046	0.823	3.65E-05	0.435	3.3	0.001	3.00E-06	
MOS6020-472	0.1	90	120	0.050	0.965	8.20E-05	0.680	4.7	0.030	9.40E-06	
MOS6020-682	0.1	80	132	0.078	1.19	1.00E-05	1.21	6.8	0.040	9.70E-06	
MOS6020-103	0.1	70	80	0.092	1.42	1.00E-05	1.45	10	0.059	9.78E-06	
MOS6020-153	0.1	60	60	0.130	1.31	1.06E-04	2.11	15	0.086	9.50E-06	
MOS6020-223	0.1	50	66	0.182	1.50	1.00E-05	4.18	22	0.130	9.80E-06	
MOS6020-333	0.1	40	110	0.290	1.51	1.00E-05	6.35	33	0.230	9.87E-06	
MOS6020-473	0.1	30	100	0.420	1.85	1.00E-05	7.54	47	0.306	9.80E-06	
MOS6020-683	0.1	20	115	0.520	1.81	1.00E-05	12.2	68	0.400	9.88E-06	
MOS6020-104	0.1	20	94	0.800	1.52	1.00E-05	16.3	100	0.680	9.87E-06	
MOS6020-154	0.1	20	240	1.28	1.94	1.00E-05	40	150	0.595	1.02E-05	
MOS6020-224	0.1	10	350	2.00	2.12	1.00E-05	80	220	0.600	1.06E-05	
MOS6020-334	0.1	10	400	2.84	1.84	1.00E-05	88	330	0.600	1.11E-05	
MOS6020-474	0.1	6	350	4.40	2.55	1.00E-05	280	470	0.600	1.43E-05	

